

Objective:

- Design a pure sine wave three-phase inverter of 2.2 Kwtt.
- The switching frequency is 50 khz. calculate the losses in the inverter and filter.
- Use PLECS to model the magnetics and give the performance table for unipolar Sine PWM and Space Vector PWM.

Software Required:

PLECS

Introduction: • Inverter is a device which convert a DC input supply voltage into symmetric AC voltage of desired magnitude and frequency at the output side. It is also known as DC-AC converter.

- Ideal and practical inverter have sinusoidal and non-sinusoidal waveforms at output respectively.
- If the input dc is a voltage source, the inverter is called a Voltage Source Inverter (VSI). One can similarly think of a Current Source Inverter (CSI), where the input to the circuit is a current source. The VSI circuit has direct control over 'output (ac) voltage' whereas the CSI directly controls 'output (ac) current'.

Classifications of inverter:

Inverter can be mainly classified into two types-

- 1) Single-phase inverter
- 2) Three-phase inverter

Three phase inverter Simulink Model: - (VSI) :

The load fed by the inverter is a resistive load with a resistance of 12.15 ohm per phase (Star Connected Load)

Considering : $V_{dc} = 230 \text{ volt}$

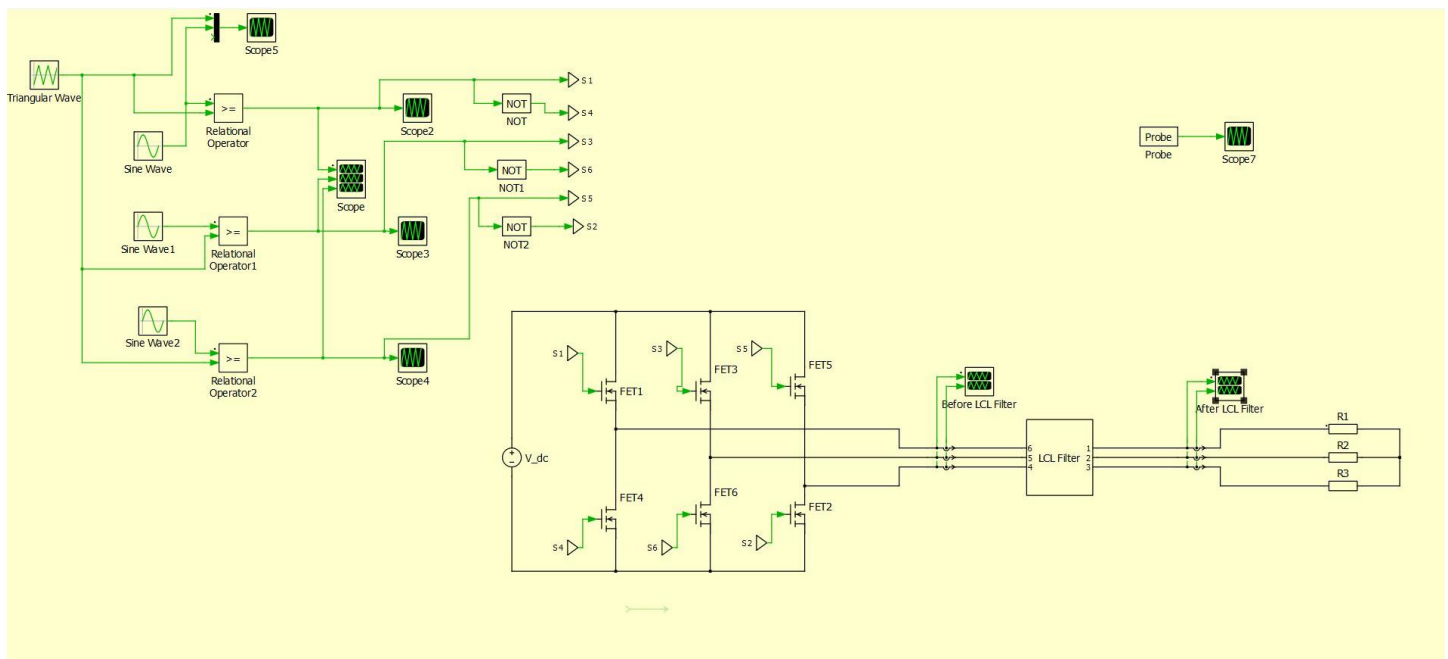


Fig: Simulation model of 3 phase inverter

Sine PWM Waveform

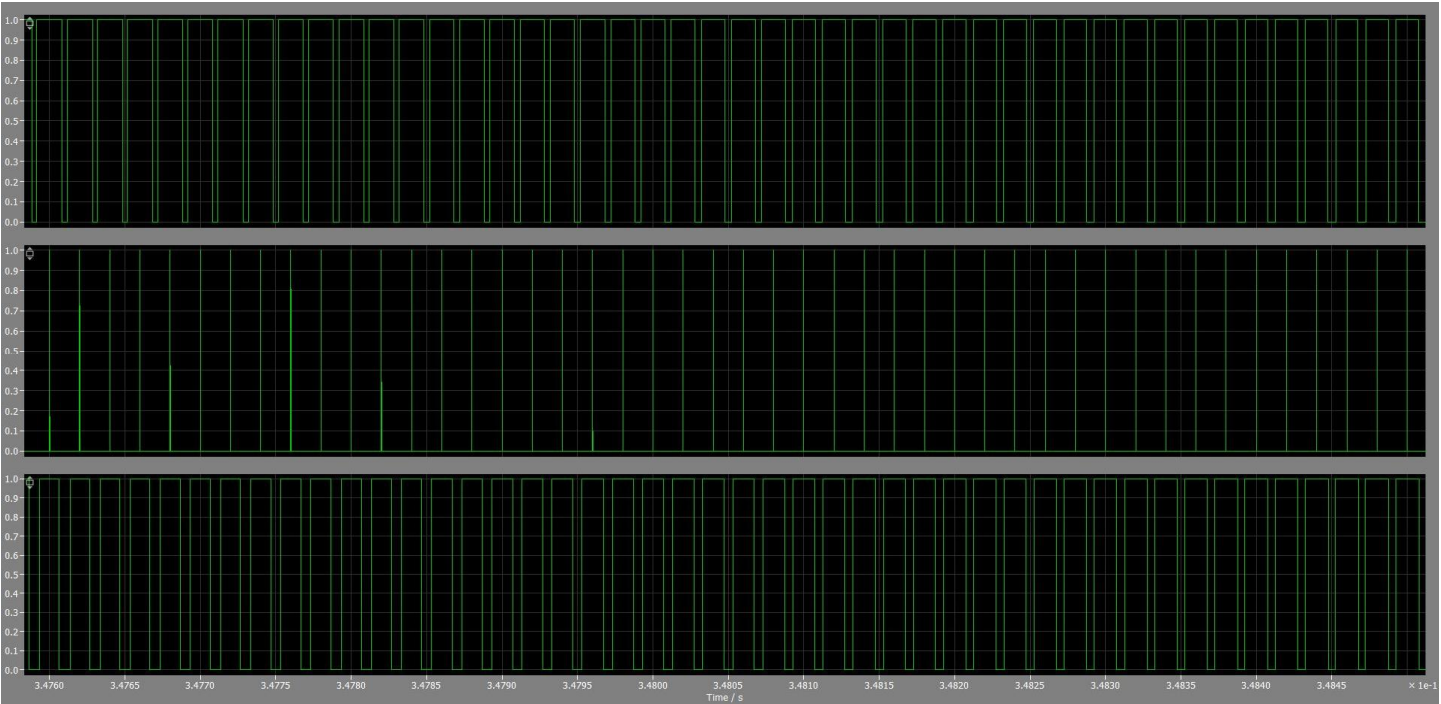


Fig: 3 phases of sine PWM

Before LCL Circuit Voltage and cuurent waveform:


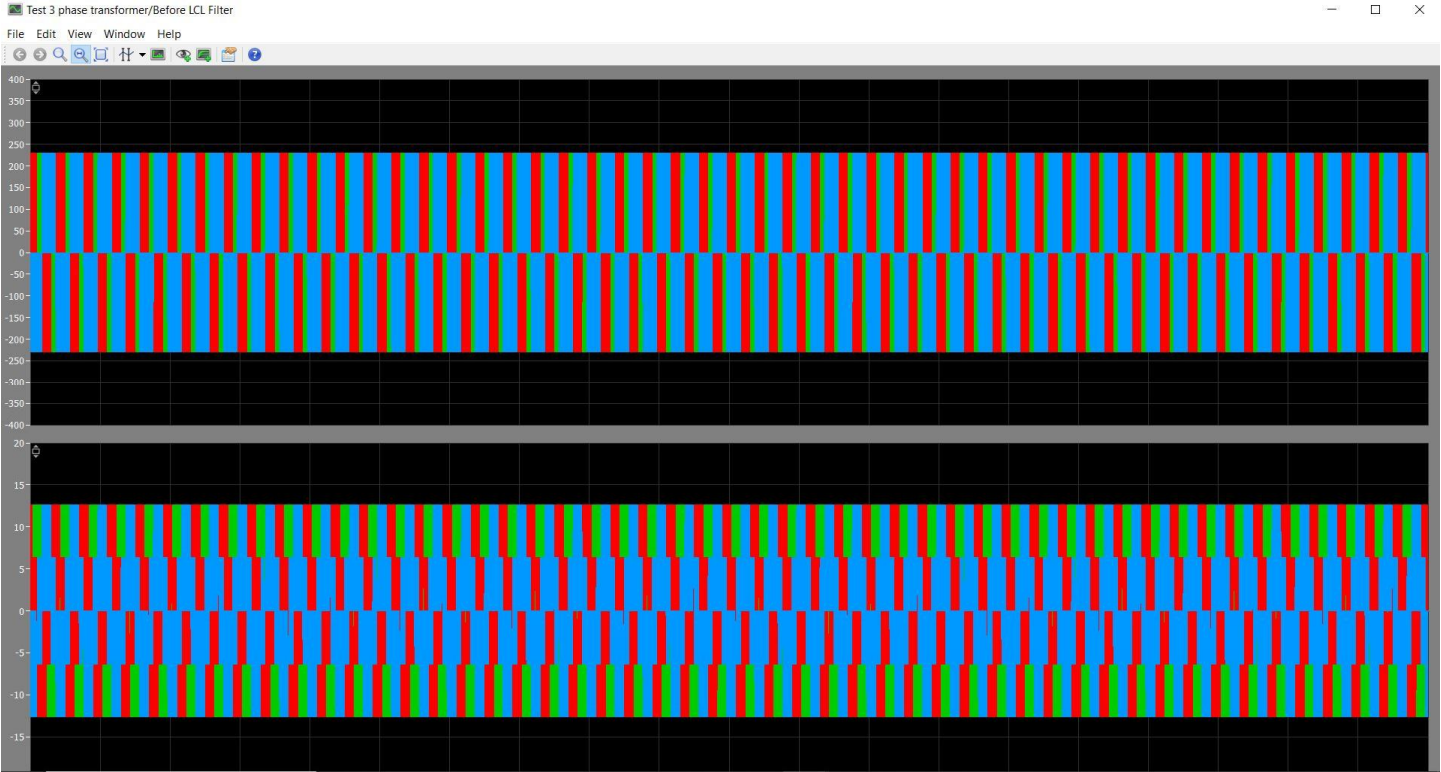


Fig: Before filter Output voltage and current waveform


Output Voltage : $V_p - V_p = 230$ volt

With Zoom

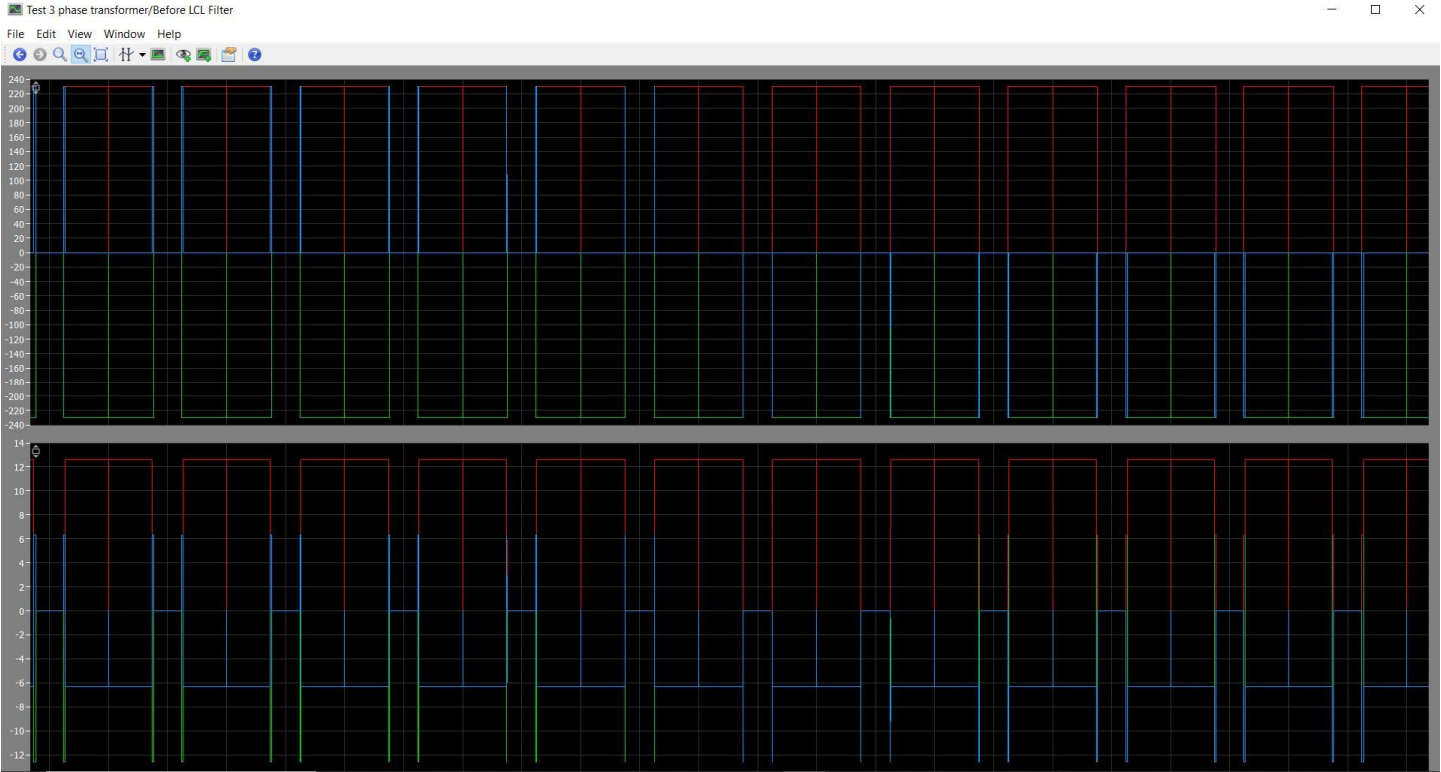

DESIGNING OF LCL FILTER:

LCL-Filter design

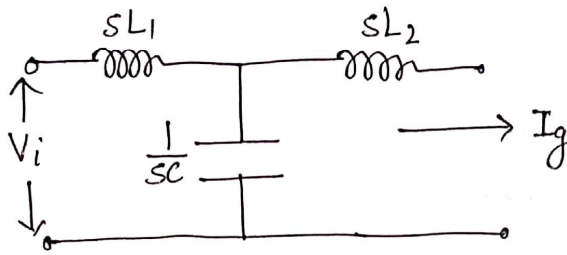

$$\frac{I_g}{V_i} = \frac{1}{s^3 L_1 L_2 C + s(L_1 + L_2)}$$

Let.

$$L_1 + L_2 = L$$
$$\& L_p = \frac{L_1 \cdot L_2}{L_1 + L_2}$$

$$\frac{I_g}{V_i} = \frac{1}{sL(1 + s^2 CL_p)}$$

$$\omega_{res} = \frac{1}{\sqrt{CL_p}}$$

Given Switching freq: $F_{sw} = 50 \text{ KHz}$.

$$\text{Resonant freq} = \frac{F_{sw}}{10} = 5 \text{ KHz} = f_{res}$$

Value of Capacitance — Let $S = 2.2 \text{ KVA}$

Let Reactive power = 5% of Rated Power.

$$Q = \frac{V^2}{1/2\pi f C} \Rightarrow$$

$$C = \frac{0.05 \times S}{V^2 \times 2 \times \pi \times f}$$

$$V_{p-p} = 230 \text{ V}$$

$$C = \frac{0.05 \times 2200/3}{230 \times 2 \times \pi \times 50}$$

$$C = 507 \text{ MF}$$

Finding Value of Inductance:

$$\frac{I_g}{V_i} = \frac{1}{sL(1+s^2L_pC)} \quad , \quad \omega_{res} = \frac{1}{\sqrt{CL_p}}$$

Putting $s = j\omega$.

$$\left| \frac{I_g}{V_i} \right| = \left| \frac{1}{\omega_{sw} \cdot L \left(1 - \frac{\omega_{sw}^2}{\omega_{res}^2} \right)} \right|$$

$$L = \left| \frac{1}{\omega_{sw} \frac{I_g(s\omega)}{V_i(s\omega)} \left(1 - \frac{\omega_{sw}^2}{\omega_{res}^2} \right)} \right|$$

$$\text{Current } I_g = \frac{2200/3}{230} = 3.18$$

$$I_g(\text{sw}) = 0.3\% \text{ of } I_g =$$

$$= 9.54 \text{ mA.}$$

$$V_i(\text{sw}) = 0.9 \text{ times of } V_g$$

$$= 0.9 \times 230$$

$$= 207 \text{ V.}$$

$$L = \frac{1}{2 \times \pi \times 50000 \times \frac{9.54 \times 10^{-3}}{207} \times \left[1 - \left(\frac{2 \times \pi \times 50000}{2 \times \pi \times 5000} \right)^2 \right]}$$

$$L = 69.76 \text{ mH}$$

$$\boxed{L = 697.6 \text{ MH}} \quad L_1 = L_2 = \frac{L}{2}$$

$$L_1 = L_2 = 348.80 \text{ MH. [Minimum Value]}$$

$$L_{\max} = \frac{0.2 \times V_{\text{in}}}{2 \times \pi \times 50 \times I}$$

$$\boxed{L_{\max} = 46 \text{ mH.}} \quad [\text{Maximum Value}].$$

$$\text{taking } L_1 = L_2 = 2.85 \text{ mH}$$

$$C = 507 \text{ MF.}$$

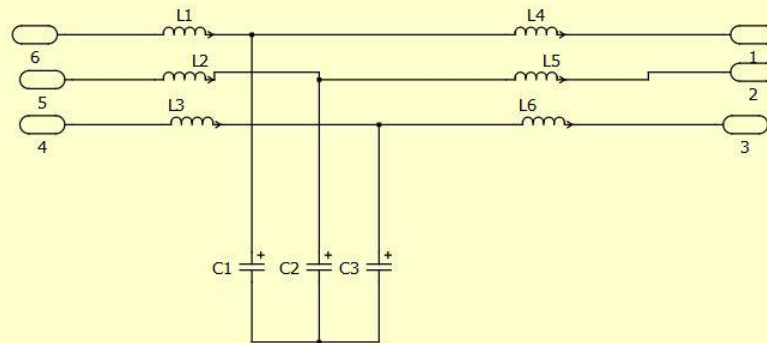


Fig: LCL filter


After calculating the value we taken;

Invetre Side : $L = 2.85 \text{ mH}$ per phase

Load Side : $L = 2.85 \text{ mH}$ per phase

Capacitor vale $C = 507 \text{ uF}$

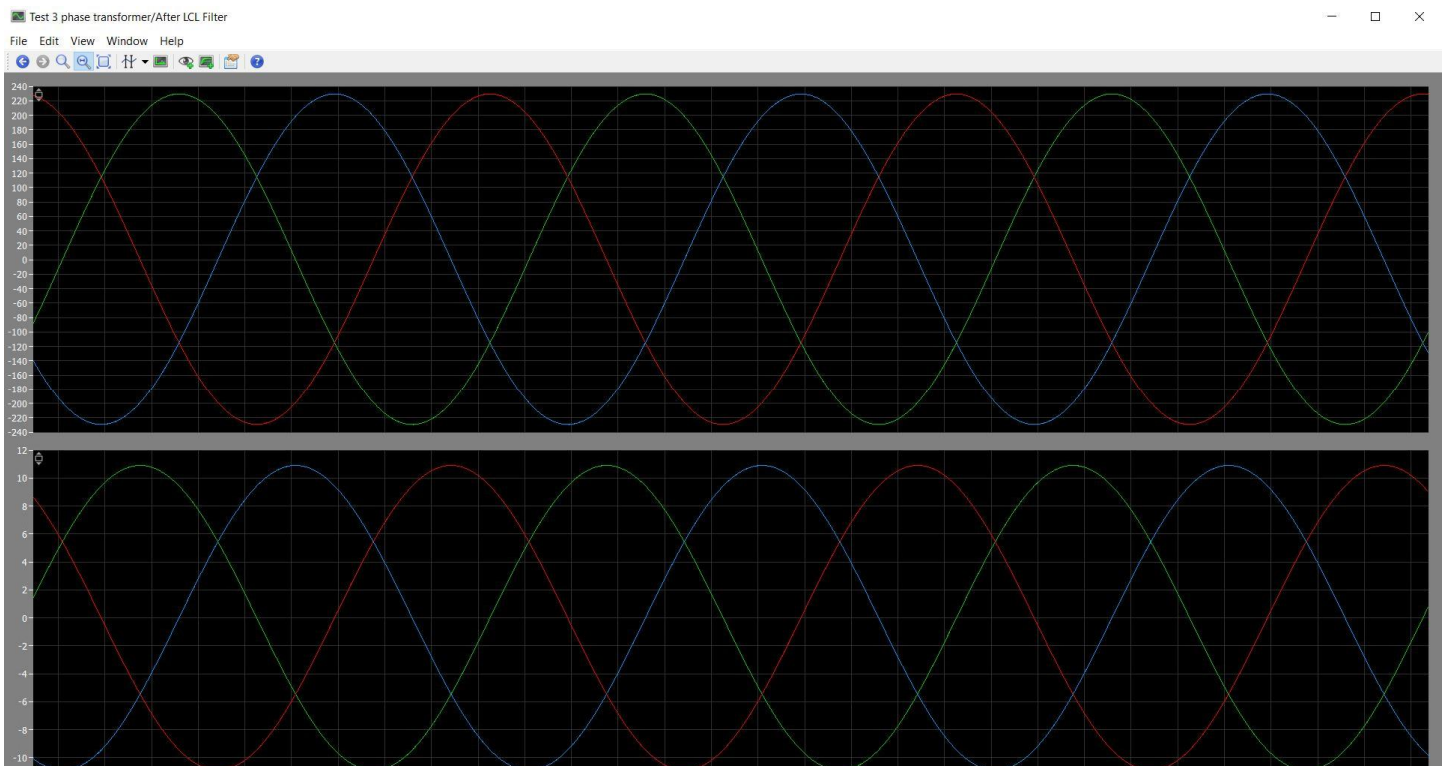With LCL output voltage and current waveform :



Maximum Output Voltage : 229.412 volt

RMS Output Voltage : 162.356 volt

Maximum Output Current :10.9013 amp

RMS Output Current : 7.7386 amp

Data					
Name		Cursor 1	Cursor 2	Max	RMS
Time		0.333335	0.666665		
Plot 1					
3ph Meter1:Measured voltage:1	✓	-82.0634	226.524	229.412	162.356
3ph Meter1:Measured voltage:2	✓	-144.499	-81.839	229.412	161.58
3ph Meter1:Measured voltage:3	✓	226.562	-144.685	229.412	162.717
Plot 2					
3ph Meter1:Measured current:1	✓	-8.46709	10.1841	10.9013	7.7386
3ph Meter1:Measured current:2	✓	-1.7129	-8.4599	10.9013	7.68463
3ph Meter1:Measured current:3	✓	10.18	-1.72418	10.9013	7.70184

Output Power:

$$P = \sqrt{3}V_{rms}I_{rms}$$
$$P = 2176.61 \text{ watt}$$

Following points may be noted from the output waveform of three phase bridge inverter with LCL Filter:

- Phase voltages have sinusoidal nature as desired.
- The line voltages represent a balanced set of three phase alternating voltages.

Losses in Switch :

Name	Cursor 1	Cursor 2	Max	Mean	RMS
Time	0.333335	0.666665			
Plot 1					
FET1:MOSFET junction temp	✓	✓	177.217	273.847	335.732
FET1:MOSFET conduction loss	✓	✓	0	0.35366	190.826
Plot 2					
FET1:MOSFET switching loss	✓	✓	0	0.000290973	9.67296e-06
Plot 3					
FET1:MOSFET switching loss	✓	✓	0	0.000290973	9.67296e-06

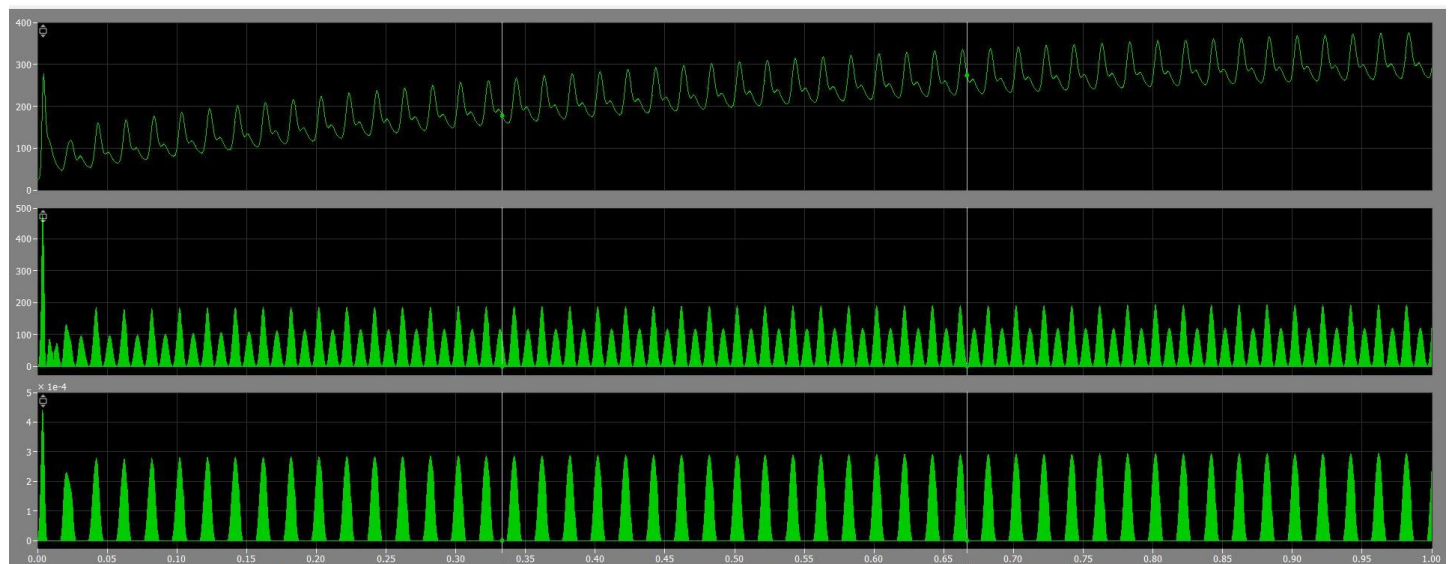


Fig:1. Switch Junction Temp, 2.Switch Conduction Loss, 3. Swticing loss

Total Loss in Inverter :
Conduction Loss: 40.46 w
Sw Loss : 9.67 uW

Conclusion:

In conclusion, the successful design and simulation of a 3-phase inverter with a 2.2 kW power rating, featuring a pure sine wave output and an LCL filter, represents a noteworthy achievement in the realm of power electronics. The integration of advanced control strategies and the inclusion of the LCL filter not only fulfill the specified power requirements but also ensure a high-quality output waveform with reduced harmonic distortion.